 


Microcoded Instruction Set Processor



The Second project of the module. To implement a Microprogrammed Instruction Set Processor in VHDL.

Introduction

This project builds on the previously implemented Register File and Datapath. Instructions are written into the memory of the processor that implement a program to demonstrate the workings of some of the instructions it can perform. The Program Counter steps through these instructions, loading them into the Instruction Register. When an instruction is to be executed, the Control Address Register points into Control Memory to the codes that need to be sent to various parts of the processor to perform the instruction. Control Memory has these codes stored for each of the instructions. Instructions contain 'opcode's which correspond to the address in Control Memory where their corresponding codes can be found.

The Program

I have written a trivial program to demonstrate the workings of some of the instructions the Processor can perform:

```
Instructions

ADI R3, R3, #3
ADD R3, R3, R3
ADI R4, R4, #1
SR  R4, R4, R4
ADD R3, R3, R3
LD  R7, Memory[R3]
NOT R3, R3
while INC R3, R3
      BNZ while
stop  B stop
```

Each of these operations is performed in the test bench of the main module, the Processor. The inputs to the processor are a Clock (Clk) and a Reset. The reset sets the registers to 0 initialises the Program Counter (PC) and the Control Address Register (CAR).

In this document, I will show this main test bench and explain the instructions as it goes on. Then I will attach the code for some of the more important components (those not already submitted) and their test benches.

Processor TestBench

```
-----  
-- Engineer:  
-- Create Date:    21:04:00 04/01/2016  
-- Module Name:    U:/decoder_3to8/processor_final_TestBench.vhd  
-- Project Name:   CS2022 Computer Architecture 2016 Project 2  
-----
```

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;
```

```
ENTITY processor_final_TestBench IS  
END processor_final_TestBench;
```

```
ARCHITECTURE behavior OF processor_final_TestBench IS
```

```
    -- Component Declaration for the Unit Under Test (UUT)
```

```
    COMPONENT processor_final  
    PORT(  
        Clk : IN  std_logic;  
        reset : IN  std_logic  
    );  
    END COMPONENT;
```

```
    --Inputs
```

```
    signal Clk : std_logic := '0';  
    signal reset : std_logic := '0';
```

```
    -- Clock period definitions
```

```
    constant Clk_period : time := 10 ns;
```

```
BEGIN
```

```
    -- Instantiate the Unit Under Test (UUT)
```

```
    uut: processor_final PORT MAP (  
        Clk => Clk,  
        reset => reset  
    );
```

```
    -- Clock process definitions
```

```
    Clk_process :process
```

```
    begin
```

```
        Clk <= '0';
```

```
        wait for Clk_period/2;
```

```
        Clk <= '1';  
        wait for Clk_period/2;  
    end process;
```

```
    -- Stimulus process
```

```
    stim_proc: process
```

```
    begin
```

```
        reset <= '1';
```

```
        wait for 100 ns;
```

```
        reset <= '0';
```


```
        wait;
```

```
    end process;
```

```
END;
```

Reset

 Upon Starting the test bench, the reset is set to 1 for 100 nano seconds to demonstrate the initialisation of the system. The PC is set to 0, the CAR (Depicted as 'data_out' in all test benches) is set to fetch (110000) and the registers are set to 0.



Please note that 'data_out' refers to the CAR's output throughout. This is the index into Control Memory.

The inside of Control Memory looks like this:

--Instruction	Address	Next Address	. MS	MC	IL	PI	PL	TD	TA	TB	MB	. FS	.MD	RW	MM	MW	Code
ADI	00	IF -> C0	001	0	0	0	0	0	0	0	1	00010	0	1	0	0	= 0xC020224
LD	01	IF -> C0	001	0	0	0	0	0	0	0	0	00000	1	1	0	0	= 0xC02000C
ST	02	IF -> C0	001	0	0	0	0	0	0	0	0	00000	0	0	0	1	= 0xC020001
INC	03	IF -> C0	001	0	0	0	0	0	0	0	0	00001	0	1	0	0	= 0xC020014
NOT	04	IF -> C0	001	0	0	0	0	0	0	0	0	01110	0	1	0	0	= 0xC0200E4
ADD	05	IF -> C0	001	0	0	0	0	0	0	0	0	00010	0	1	0	0	= 0xC020024
LRI	06	LRI2-> 86	001	0	0	0	0	0	0	0	0	00000	1	1	0	0	= 0x862000C
SR	07	SR2 -> 87	111	0	0	0	0	1	0	0	0	00000	0	1	0	0	= 0x87E1004
BEQ	09	B -> 30	100	0	0	0	1	1	1	1	0	10000	0	1	0	0	= 0x0081D04
Catch	0A	IF -> C0	001	0	0	0	0	0	0	0	0	00000	0	0	0	0	= 0xC020000
BNZ	0B	B -> 30	111	0	0	0	0	0	0	0	0	00000	0	0	0	0	= 0x30E0000
Catch	0C	IF -> C0	001	0	0	0	0	0	0	0	0	00000	0	0	0	0	= 0xC020000
CMP	0D	IF -> C0	001	0	0	0	0	1	0	0	0	00101	0	1	0	0	= 0xC021054
LR	29	IF -> C0	001	0	0	0	0	0	0	0	0	00000	1	1	0	0	= 0xC02000C
B	30	IF -> C0	001	0	0	0	1	0	0	0	0	00000	0	0	0	0	= 0xC022000
LRI2	86	IF -> C0	001	0	0	0	0	0	1	0	0	00000	1	1	0	0	= 0xC02080C
SR2	87	SR3 -> 89	001	0	0	0	0	0	0	0	0	10100	0	1	0	0	= 0x8820144
SR3	88	SR2 -> 87	100	0	0	0	0	1	1	0	0	00110	0	1	0	0	= 0x8781864
Catch	89	IF -> C0	001	0	0	0	0	0	0	0	0	00000	0	0	0	0	= 0xC020000
IF	C0	EXO -> C1	000	0	1	1	0	0	0	0	0	00000	0	0	1	0	= 0xC10C002
EXO	C1	-- -> 00	001	1	0	0	0	0	0	0	0	00000	0	0	0	0	= 0x0030000

A useful key

You can note that some instructions take longer than others and have a few corresponding lines in control memory, such as Shift Right and Load Immediate Register which make use of the temporary register, R8.

The full code for the Control Memory and Memory will be attached later in the document but here is view that is helpful to keep in mind when looking through the test bench:

Start of Control Memory

```
memory_m: process(IN_CAR)
variable control_mem : mem_array:= (

X"C020224", -- 0x00 ADI: Add immediate constant
X"C02000C", -- 0x01 LD: Load
X"C020001", -- 0x02 ST: Store
X"C020014", -- 0x03 INC: Increment
X"C0200E4", -- 0x04 NOT: Not
X"C020024", -- 0x05 ADD: Add
X"862000C", -- 0x06 LRI: Load into immediate register Micro operation 1
X"87E1004", -- 0x07 SR: Shift Right Micro-operation 1
X"C020000", -- 0x08 Catch (to fall through to if shifted right by zero)
X"3080000", -- 0x09 BEQ: Branch if equal
X"C020000", -- 0x0A Catch (to fall through to if branch not taken)
X"30E0000", -- 0x0B BNZ: Branch if not zero
X"C020000", -- 0x0C Catch (to fall through to if branch not taken)
X"C021054", -- 0x0D CMP: Compare
X"0000000", -- 0x0E
X"0000000", -- 0x0F
```

Start of Memory

```
variable data_mem : mem_array := (


--          PC          Instructions          Pseudocode          Codewords
--          Opcode DR  SA  SB

X"00DB", --0000          ADI R3, R3, #3          R3 = (0 + 3) = 3          0000000 011 011 011
X"0ADB", --0001          ADD R3, R3, R3          R3 = (3 + 3) = 6          0000101 011 011 011
X"0121", --0010          ADI R4, R4, #1          R4 = (0 + 1) = 1          0000000 100 100 001
X"0F24", --0011          SR R4, R4, R4          R4 = (1 >> 1) = 0x8000    0000111 100 100 100
X"0ADB", --0100          ADD R3, R3, R3          R3 = (6 + 6) = 12        0000101 011 011 011
X"03D8", --0101          LD R7, Memory[R3]          R7 = Memory[12] = 0x00FF  0000001 111 011 000
X"08D8", --0110          NOT R3, R3          R3 = (~12) = 0xFFFF3     0000100 011 011 000
X"06D8", --0111          while INC R3, R3          4x(R3 = R3 + 1) = 0       0000011 011 011 000
X"17C6", --1000          BNZ while          0001011 111 000 110
X"3A00", --1001          stop B stop          0011101 000 000 000
X"0000", --          State now = [R3==0 R4==0x8000 R7==0xFF]
X"0000", --
X"00FF", --(Memory[12])
```

The Hex values stored in memory correspond to the binary of the codewords for the instructions.

ADI R3, R3, #3

 This adds the constant value 3 from SB to the value in R3 (0) and places it into R3.



Address in
Control Memory


Before

After

PC points to next
instruction in memory

ADI R3, R3, R3

 This adds the value in R3 to itself and places it in R3.



Address in
Control Memory


Before

After

PC points to next
instruction in memory

ADI R4, R4, #1

 Adds the value in R4 (0) with the constant value 1 and places the result in R4.



Address in
Control Memory


Before

After

PC points to next
instruction in memory

SR R4, R4, #1

 This shifts the value in R4 by one bit to the right.



Address of
different codes for
shift in Control
Memory

Before


After

Number of times to
shift by stored in R8

PC points to next
instruction in memory

ADD R3, R3, R3

 This addition is once again performed. (In order to help the future demonstration of the Load instruction)



Address in
Control Memory


Before

After

PC points to next
instruction in memory

LD R7, Memory[R3]

 This instruction loads the value in memory indexed by the value in the register R3 into R7. (0xFF)



PC points to next
instruction in memory


Before

After

Address in
Control Memory

NOT R3, R3

 This instruction negates the value in R3 and places it into R3.



PC points to next instruction in memory


Before

Address in Control Memory

After

INC R3, R3

 The value in R3 is now incremented and then placed back into R3.



PC points to next instruction in memory


Before

Address in Control Memory

After

BNZ while

 This branches to the the current program counter value offsetted by the bit specified in [6..4] and [2..0] in the instruction when the Zero Flag is not set. This can be seen by the continuous incrementing of the value in R3 until it becomes 0.



PC points again to a previous instruction

After incrementing for a second time inside the loop

Components and Test Benches

Processor Behavioural

```
-- Engineer:
-- Create Date:    12:56:58 04/01/2016
-- Module Name:    processor - Behavioral
-- Project Name:

-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity processor_final is
    Port(
        Clk : in STD_LOGIC;
        reset : in STD_LOGIC
    );
end processor_final;

architecture Behavioral of processor_final is

    COMPONENT Microprogrammed_control is
        Port ( instruction_in : in STD_LOGIC_VECTOR (15 downto 0);
              reset : in STD_LOGIC;
              V : in STD_LOGIC;
              C : in STD_LOGIC;
              N : in STD_LOGIC;
              Z : in STD_LOGIC;
              Clk : in STD_LOGIC;
              pc_out : out STD_LOGIC_VECTOR (15 downto 0);
              DR : out STD_LOGIC_VECTOR (2 downto 0);
              SA : out STD_LOGIC_VECTOR (2 downto 0);
              SB : out STD_LOGIC_VECTOR (2 downto 0);
              TD : out STD_LOGIC;
              TA : out STD_LOGIC;
              TB : out STD_LOGIC;
              MB : out STD_LOGIC;
              FS : out STD_LOGIC_VECTOR (4 downto 0);
              MD : out STD_LOGIC;
              RW : out STD_LOGIC;
              MM : out STD_LOGIC;
              MW : out STD_LOGIC);
    end COMPONENT;

    COMPONENT last_data_path is
        Port ( PC : in STD_LOGIC_VECTOR (15 downto 0);
              data_in : in STD_LOGIC_VECTOR (15 downto 0);
              DR : in STD_LOGIC_VECTOR (2 downto 0);
              SA : in STD_LOGIC_VECTOR (2 downto 0);
              SB : in STD_LOGIC_VECTOR (2 downto 0);
              TD : in STD_LOGIC;
              TA : in STD_LOGIC;
              TB : in STD_LOGIC;
              Clk : in STD_LOGIC;
              reset : in STD_LOGIC;
              FS : in STD_LOGIC_VECTOR (4 downto 0);
              RW : in STD_LOGIC;
              MB : in STD_LOGIC;
              MM : in STD_LOGIC;
              MD : in STD_LOGIC;
              data_out : out STD_LOGIC_VECTOR (15 downto 0);
              address_out : out STD_LOGIC_VECTOR (15 downto 0);
              V : out STD_LOGIC;
              C : out STD_LOGIC;
              N : out STD_LOGIC;
              Z : out STD_LOGIC);
    end COMPONENT;

    COMPONENT memory_512
    PORT(
        address : IN std_logic_vector(15 downto 0);
        write_data : IN std_logic_vector(15 downto 0);
        Clk : IN std_logic;
        MemWrite : IN std_logic;
        read_data : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --signals
    signal V_signal : std_logic;
    signal C_signal : std_logic;
    signal N_signal : std_logic;
    signal Z_signal : std_logic;
    signal TD_signal : std_logic;
    signal TA_signal : std_logic;
    signal TB_signal : std_logic;
    signal MB_signal : std_logic;
    signal MD_signal : std_logic;
    signal RW_signal : std_logic;
    signal MM_signal : std_logic;
    signal MW_signal : std_logic;
    signal DR_signal : std_logic_vector(2 downto 0);
    signal SA_signal : std_logic_vector(2 downto 0);
    signal SB_signal : std_logic_vector(2 downto 0);
    signal FS_signal : std_logic_vector(4 downto 0);
    signal datapath_address_out : std_logic_vector(15 downto 0);
    signal datapath_data_out : std_logic_vector(15 downto 0);
    signal memory_data_out : std_logic_vector(15 downto 0);
    signal micro_pc_out : std_logic_vector(15 downto 0);

begin
    micro_control : Microprogrammed_control PORT MAP (
        instruction_in => memory_data_out,
        reset => reset,
        V => V_signal,
        C => C_signal,
        N => N_signal,
        Z => Z_signal,
        Clk => Clk,
        pc_out => micro_pc_out,
        DR => DR_signal,
        SA => SA_signal,
        SB => SB_signal,
        TD => TD_signal,
        TA => TA_signal,
        TB => TB_signal,
        MB => MB_signal,
        FS => FS_signal,
        MD => MD_signal,
        RW => RW_signal,
        MM => MM_signal,
        MW => MW_signal
    );

    data_path : last_data_path PORT MAP (
        PC => micro_pc_out,
        data_in => memory_data_out,
        DR => DR_signal,
        SA => SA_signal,
        SB => SB_signal,
        TD => TD_signal,
        TA => TA_signal,
        TB => TB_signal,
        Clk => Clk,
        reset => reset,
        FS => FS_signal,
        RW => RW_signal,
        MB => MB_signal,
        MM => MM_signal,
        MD => MD_signal,
        data_out => datapath_data_out,
        address_out => datapath_address_out,
        V => V_signal,
        C => C_signal,
        N => N_signal,
        Z => Z_signal
    );

    mem : memory_512 PORT MAP (
        address => datapath_address_out,
        write_data => datapath_data_out,
        Clk => Clk,
        MemWrite => MW_signal,
        read_data => memory_data_out
    );
end Behavioral;
```

Processor Test Bench

```
-----  
-- Engine  
-- Create Date:      21:04:00 04/01/2016  
-- Module Name:      U:/decoder_3to8/processor_final_TestBench.vhd  
-- Project Name:     CS2022 Computer Architecture 2016 Project 2  
-----  
  
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
  
ENTITY processor_final_TestBench IS  
END processor_final_TestBench;  
  
ARCHITECTURE behavior OF processor_final_TestBench IS  
  
    -- Component Declaration for the Unit Under Test (UUT)  
  
    COMPONENT processor_final  
    PORT(  
        Clk : IN  std_logic;  
        reset : IN  std_logic  
    );  
    END COMPONENT;  
  
    --Inputs  
    signal Clk : std_logic := '0';  
    signal reset : std_logic := '0';  
  
    -- Clock period definitions  
    constant Clk_period : time := 10 ns;  
  
BEGIN  
  
    -- Instantiate the Unit Under Test (UUT)  
    uut: processor_final PORT MAP (  
        Clk => Clk,  
        reset => reset  
    );  
  
    -- Clock process definitions  
    Clk_process :process  
    begin  
        Clk <= '0';  
        wait for Clk_period/2;  
        Clk <= '1';  
        wait for Clk_period/2;  
    end process;  
  
    -- Stimulus process  
    stim_proc: process  
    begin  
        reset <= '1';  
        wait for 100 ns;  
        reset <= '0';  
        wait;  
    end process;  
  
END;
```

Microprogrammed Control Behavioural

```

-- Engineer
-- Create Date:      22:35:59 03/30/2016
-- Module Name:      Microprogrammed_control - Behavioral
-- Project Name:      CS2022 Computer Architecture 2016 Project 2
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Microprogrammed_control is
    Port ( instruction_in : in  STD_LOGIC_VECTOR (15 downto 0);
          reset : in STD_LOGIC;
          V : in  STD_LOGIC;
          C : in  STD_LOGIC;
          N : in  STD_LOGIC;
          Z : in  STD_LOGIC;
          Clk : in STD_LOGIC;
          pc_out : out  STD_LOGIC_VECTOR (15 downto 0);
          DR : out  STD_LOGIC_VECTOR (2 downto 0);
          SA : out  STD_LOGIC_VECTOR (2 downto 0);
          SB : out  STD_LOGIC_VECTOR (2 downto 0);
          TD : out  STD_LOGIC;
          TA : out  STD_LOGIC;
          TB : out  STD_LOGIC;
          MB : out  STD_LOGIC;
          FS : out  STD_LOGIC_VECTOR (4 downto 0);
          MD : out  STD_LOGIC;
          RW : out  STD_LOGIC;
          MM : out  STD_LOGIC;
          MW : out  STD_LOGIC);
end Microprogrammed_control;

architecture Behavioral of Microprogrammed_control is

    COMPONENT PC
        PORT(
            Extend : IN  std_logic_vector(15 downto 0);
            reset : IN  std_logic;
            PI : IN  std_logic;
            S0 : IN  std_logic;
            S1 : IN  std_logic;
            S2 : IN  std_logic;
            line_out : OUT std_logic
        );
    END COMPONENT;

    COMPONENT Extend
        PORT(
            DR : IN  std_logic_vector(2 downto 0);
            SB : IN  std_logic_vector(2 downto 0);
            extension : OUT std_logic_vector(15 downto 0)
        );
    END COMPONENT;

    COMPONENT IR
        PORT(
            data_in : IN  std_logic_vector(15 downto 0);
            IL : IN  std_logic;
            Clk : IN  std_logic;
            Opcode : OUT  std_logic_vector(6 downto 0);
            DR : OUT  std_logic_vector(2 downto 0);
            SA : OUT  std_logic_vector(2 downto 0);
            SB : OUT  std_logic_vector(2 downto 0)
        );
    END COMPONENT;

    COMPONENT mux_2_to_1_8bit
        PORT(
            S : IN  std_logic;
            In0 : IN  std_logic_vector(7 downto 0);
            In1 : IN  std_logic_vector(7 downto 0);
            Z : OUT  std_logic_vector(7 downto 0)
        );
    END COMPONENT;

    COMPONENT CAR
        PORT(
            data_in : IN  std_logic_vector(7 downto 0);
            reset : IN  std_logic;
            Clk : IN  std_logic;
            Con : IN  std_logic;
            data_out : OUT  std_logic_vector(7 downto 0)
        );
    END COMPONENT;

    COMPONENT control_memory
        PORT(
            MW : OUT  std_logic;
            MM : OUT  std_logic;
            RW : OUT  std_logic;
            MD : OUT  std_logic;
            FS : OUT  std_logic_vector(4 downto 0);
            MB : OUT  std_logic;
            TB : OUT  std_logic;
            TA : OUT  std_logic;
            TD : OUT  std_logic;
            PL : OUT  std_logic;
            PI : OUT  std_logic;
            IL : OUT  std_logic;
            MC : OUT  std_logic;
            MS : OUT  std_logic_vector(2 downto 0);
            NA : OUT  std_logic_vector(7 downto 0);
            IN_CAR : IN  std_logic_vector(7 downto 0)
        );
    END COMPONENT;

    --signals
    signal MC : std_logic;
    signal IL : std_logic;
    signal PI : std_logic;
    signal PL : std_logic;

    signal not_Z : std_logic;
    signal not_C : std_logic;
    signal mux_s_out : std_logic;
    signal MS : std_logic_vector(2 downto 0);
    signal DR_signal : std_logic_vector(2 downto 0);
    signal SA_signal : std_logic_vector(2 downto 0);
    signal SB_signal : std_logic_vector(2 downto 0);
    signal NA : std_logic_vector(7 downto 0);
    signal mux_c_out : std_logic_vector(7 downto 0);
    signal car_out : std_logic_vector(7 downto 0);
    signal extend_out : std_logic_vector(15 downto 0);
    signal ir_opcode_out : std_logic_vector(6 downto 0);

begin

    extender : Extend PORT MAP (
        DR => DR_signal,
        SB => SB_signal,
        extension => extend_out
    );

    program_counter : PC PORT MAP (
        Extend => extend_out,
        reset => reset,
        Clk => Clk,
        PL => PL,
        PI => PI,
        PC_out => pc_out
    );

    mux_s : mux_2_to_1_8bit PORT MAP (
        A(0) => '0',
        A(1) => '1',
        A(2) => C,
        A(3) => V,
        A(4) => Z,
        A(5) => N,
        A(6) => not_C,
        A(7) => not_Z,
        S0 => MS(0),
        S1 => MS(1),
        S2 => MS(2),
        line_out => mux_s_out
    );

    instruction_register : IR PORT MAP (
        data_in => instruction_in,
        IL => IL,
        Clk => Clk,
        Opcode => ir_opcode_out,
        DR => DR_signal,
        SA => SA_signal,
        SB => SB_signal
    );

    mux_c : mux_2_to_1_8bit PORT MAP (
        In0 => NA,
        In1(7) => '0',
        In1(6 downto 0) => ir_opcode_out,
        S => MC,
        Z => mux_c_out
    );

    control_address_register : CAR PORT MAP (
        data_in => mux_c_out,
        reset => reset,
        Clk => Clk,
        Con => mux_s_out,
        data_out => car_out
    );

    control_me : control_memory PORT MAP (
        MW => MW,
        MM => MM,
        RW => RW,
        MD => MD,
        FS => FS,
        MB => MB,
        TB => TB,
        TA => TA,
        TD => TD,
        PL => PL,
        PI => PI,
        IL => IL,
        MC => MC,
        MS => MS,
        NA => NA,
        IN_CAR => car_out
    );

    DR <= DR_signal;
    SB <= SB_signal;
    SA <= SA_signal;
    not_C <= not C;
    not_Z <= not Z;
end Behavioral;

```

Microprogrammed Control Test Bench

```

-- Company
-- Create Date:    13:52:32 04/01/2016
-- Module Name:    U:/decoder_3to8/Microprogrammed_control_TestBench.vhd
-- Project Name:    CS2022 Computer Architecture 2016 Project 2
--
--
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Microprogrammed_control_TestBench IS
END Microprogrammed_control_TestBench;

ARCHITECTURE behavior OF Microprogrammed_control_TestBench IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT Microprogrammed_control
    PORT(
        instruction_in : IN  std_logic_vector(15 downto 0);
        reset          : IN  std_logic;
        V              : IN  std_logic;
        C              : IN  std_logic;
        N              : IN  std_logic;
        Z              : IN  std_logic;
        Clk             : IN  std_logic;
        pc_out          : OUT std_logic_vector(15 downto 0);
        DR              : OUT std_logic_vector(2 downto 0);
        SA              : OUT std_logic_vector(2 downto 0);
        SB              : OUT std_logic_vector(2 downto 0);
        TD              : OUT std_logic;
        TA              : OUT std_logic;
        TB              : OUT std_logic;
        MB              : OUT std_logic;
        FS              : OUT std_logic_vector(4 downto 0);
        MD              : OUT std_logic;
        RW              : OUT std_logic;
        MM              : OUT std_logic;
        MW              : OUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal instruction_in : std_logic_vector(15 downto 0) := (others => '0');
    signal reset          : std_logic := '0';
    signal V              : std_logic := '0';
    signal C              : std_logic := '0';
    signal N              : std_logic := '0';
    signal Z              : std_logic := '0';
    signal Clk            : std_logic := '0';

    --Outputs
    signal pc_out : std_logic_vector(15 downto 0);
    signal DR     : std_logic_vector(2 downto 0);
    signal SA     : std_logic_vector(2 downto 0);
    signal SB     : std_logic_vector(2 downto 0);
    signal TD     : std_logic;
    signal TA     : std_logic;
    signal TB     : std_logic;
    signal MB     : std_logic;
    signal FS     : std_logic_vector(4 downto 0);
    signal MD     : std_logic;
    signal RW     : std_logic;
    signal MM     : std_logic;
    signal MW     : std_logic;

    -- Clock period definitions
    constant Clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Microprogrammed_control PORT MAP (
        instruction_in => instruction_in,
        reset          => reset,
        V              => V,
        C              => C,
        N              => N,
        Z              => Z,
        Clk            => Clk,
        pc_out         => pc_out,
        DR             => DR,
        SA             => SA,
        SB             => SB,
        TD             => TD,
        TA             => TA,
        TB             => TB,
        MB             => MB,
        FS             => FS,
        MD             => MD,
        RW             => RW,
        MM             => MM,
        MW             => MW
    );

    -- Clock process definitions
    Clk_process : process
    begin
        Clk <= '0';
        wait for Clk_period/2;
        Clk <= '1';
        wait for Clk_period/2;
    end process;

    stim_proc: process
    begin
        reset <= '1';
        wait for 20 ns;

        -- Testing instruction = 1101001000110111
        reset <= '0';
        instruction_in <= x"D237";
        -- output should be
        -- pc_0000000000000001
        -- dr 000
        -- sa 110
        -- sb 111
        -- td 0
        -- ta 0
        -- tb 0
        -- mb 0
        -- fs 00000
        -- md 0
        -- rw 0
        -- mm 0
        -- mw 0

        wait;
    end process;
end;

```



Data Path Behavioural

```
-- Engineer:
-- Create Date:    20:05:20 03/15/2016
-- Module Name:    data_path_16bit - Behavioral
-- Project Name:   CS2022 Computer Architecture 2016 Project 2
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity data_path_16bit is
    Port ( data_in : in  STD_LOGIC_VECTOR (15 downto 0);
          constant_in : in  STD_LOGIC_VECTOR (15 downto 0);
          control_word : in  STD_LOGIC_VECTOR (16 downto 0);
          data_out : out  STD_LOGIC_VECTOR (15 downto 0);
          address_out : out  STD_LOGIC_VECTOR (15 downto 0);
          Clk : in  STD_LOGIC;
          V : out  STD_LOGIC;
          C : out  STD_LOGIC;
          N : out  STD_LOGIC;
          Z : out  STD_LOGIC);
end data_path_16bit;
```

architecture Behavioral of data_path_16bit is

```
    COMPONENT new_reg_file
    PORT(
        des_sel : IN  std_logic_vector(2 downto 0);
        a_sel : IN  std_logic_vector(2 downto 0);
        b_sel : IN  std_logic_vector(2 downto 0);
        load_enable : IN  std_logic;
        Clk : IN  std_logic;
        d_data : IN  std_logic_vector(15 downto 0);
        a_data : OUT  std_logic_vector(15 downto 0);
        b_data : OUT  std_logic_vector(15 downto 0)
    );
    END COMPONENT;
```

```
    COMPONENT functional_unit_16bit
    PORT(
        FSS : IN  std_logic_vector(4 downto 0);
        A : IN  std_logic_vector(15 downto 0);
        B : IN  std_logic_vector(15 downto 0);
        F : OUT  std_logic_vector(15 downto 0);
        V : OUT  std_logic;
        C : OUT  std_logic;
        N : OUT  std_logic;
        Z : OUT  std_logic
    );
    END COMPONENT;
```

```
    COMPONENT mux_2_16bit
    PORT(
        S : IN  std_logic;
        In0 : IN  std_logic_vector(15 downto 0);
        In1 : IN  std_logic_vector(15 downto 0);
        Z : OUT  std_logic_vector(15 downto 0)
    );
    END COMPONENT;
```

```
--signals
signal Cout : std_logic;
signal Vout : std_logic;
signal b_to_func : std_logic_vector(15 downto 0);
signal func_out : std_logic_vector(15 downto 0);
signal d_data : std_logic_vector(15 downto 0);
signal a_data : std_logic_vector(15 downto 0);
signal b_data : std_logic_vector(15 downto 0);
```

```
begin
    func_unit: functional_unit_16bit PORT MAP (
        FSS => control_word(6 downto 2),
        A => a_data,
        B => b_to_func,
        F => func_out,
        V => V,
        C => C,
        N => N,
        Z => Z
    );
```

```
    reg_file: new_reg_file PORT MAP (
        des_sel => control_word(16 downto 14),
        a_sel => control_word(13 downto 11),
        b_sel => control_word(10 downto 8),
        load_enable => control_word(0),
        Clk => Clk,
        d_data => d_data,
        a_data => a_data,
        b_data => b_data
    );
```

```
    mux_d: mux_2_16bit PORT MAP (
        S => control_word(1),
        In0 => func_out,
        In1 => data_in,
        Z => d_data
    );
```

```
    mux_b: mux_2_16bit PORT MAP (
        S => control_word(7),
        In0 => b_data,
        In1 => constant_in,
        Z => b_to_func
    );
```

```
    address_out <= a_data;
    data_out <= b_to_func;
```

```
end Behavioral;
```

Data Path Test Bench

```

-- Engineer
-- Create Date:    21:12:26 03/15/2016
-- Module Name:    U:/decoder_3to8/data_path_TestBench.vhd
-- Project Name:   CS2022 Computer Architecture 2016 Project 2
-- VHDL Test Bench Created by ISE for module: data_path_16bit

```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

```

```

ENTITY data_path_TestBench IS
END data_path_TestBench;

```

```

ARCHITECTURE behavior OF data_path_TestBench IS

```

```

    -- Component Declaration for the Unit Under Test (UUT)

```

```

    COMPONENT data_path_16bit
    PORT(
        data_in   : IN  std_logic_vector(15 downto 0);
        constant_in : IN  std_logic_vector(15 downto 0);
        control_word : IN  std_logic_vector(16 downto 0);
        Clk       : IN  std_logic;
        data_out  : OUT std_logic_vector(15 downto 0);
        address_out : OUT std_logic_vector(15 downto 0);
        V         : OUT std_logic;
        C         : OUT std_logic;
        N         : OUT std_logic;
        Z         : OUT std_logic
    );
    END COMPONENT;

```

```

--Inputs
signal data_in   : std_logic_vector(15 downto 0) := (others => '0');
signal constant_in : std_logic_vector(15 downto 0) := (others => '0');
signal control_word : std_logic_vector(16 downto 0) := (others => '0');
signal Clk       : std_logic := '0';

```

```

--Outputs
signal data_out : std_logic_vector(15 downto 0);
signal address_out : std_logic_vector(15 downto 0);
signal V         : std_logic;
signal C         : std_logic;
signal N         : std_logic;
signal Z         : std_logic;

```

```

-- Clock period definitions
constant Clk_period : time := 10 ns;

```

BEGIN

```

-- Instantiate the Unit Under Test (UUT)
uut: data_path_16bit PORT MAP (
    data_in => data_in,
    constant_in => constant_in,
    control_word => control_word,
    data_out => data_out,
    address_out => address_out,
    Clk => Clk,
    V => V,
    C => C,
    N => N,
    Z => Z
);

```

```

-- Clock process definitions
Clk_process :process
begin
    Clk <= '0';
    wait for Clk_period/2;
    Clk <= '1';
    wait for Clk_period/2;
end process;

```

-- Stimulus process

```

stim_proc: process
begin
    --Load 0x8003 into reg5
    --101 000 000 0 00000 1 1
    data_in <= x"8003";
    control_word <= "101000000000000011";
    constant_in <= x"0000";
    wait for 100 ns;

    --Load 0x8002 into reg4

```

```

--Load 0x8002 into reg4
--100 000 000 0 00000 1 1
data_in <= x"8002";
control_word <= "100000000000000011";
constant_in <= x"0000";
wait for 100 ns;

```

```

--Add the values in reg4 and reg5 and place in reg7
--111 101 100 0 00010 0 1
data_in <= x"0000";
control_word <= "11110110000001001";
constant_in <= x"0000";
wait for 100 ns;

```

```

--Display the answer (0x8003+0x8002 = 0x5) by setting address_out to the value in reg7
--000 111 000 1 00010 0 0
data_in <= x"0000";
control_word <= "000111000100000000";
constant_in <= x"0000";
wait for 100 ns;

```

```

--Add the value in reg4 to 0x4 and place in reg7
--111 100 000 1 00010 0 1
data_in <= x"0000";
control_word <= "11110000010001001";
constant_in <= x"0004";
wait for 100 ns;



```

```

--Display the answer (0x8002+0x4 = 0x8006) by setting address_out to the value in reg7
--000 111 000 1 00000 0 0
data_in <= x"0000";
control_word <= "000111000100000000";
constant_in <= x"0000";
wait;
end process;

```

END;

  

Memory Behavioural

```

-----
-- Engineer:
-- Create Date:    17:03:19 03/29/2016
-- Module Name:    memory_S12 - Behavioral
-- Project Name:    CS2022 Computer Architecture 2016 Project 2
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.ALL;

entity memory_S12 is
    Port ( address : in  STD_LOGIC_VECTOR (15 downto 0);
          write_data : in  STD_LOGIC_VECTOR (15 downto 0);
          Clk : in  STD_LOGIC;
          MemWrite : in  STD_LOGIC;
          read_data : out  STD_LOGIC_VECTOR (15 downto 0));
end memory_S12;

architecture Behavioral of memory_S12 is

    type mem_array is array(0 to 511) of std_logic_vector(15 downto 0);
    -- define type, for memory arrays
    signal snl : unsigned(15 downto 0);

begin
    snl <= unsigned(address);
    mem_process: process (address, write_data, Clk)
    -- initialize data memory, X denotes hexadecimal number
    variable data_mem : mem_array := (
        --
        --
        PC          Instructions          Pseudocode          Codewords          Hex
        Opcode DR  SA  SB
        X"000B", --0000      ADI R3, R3, #3      R3 = (0 + 3) = 3      0000000 011 011 011      000B
        X"0AD8", --0001      ADD R3, R3, R3      R3 = (3 + 3) = 6      0000101 011 011 011      0AD8
        X"0121", --0010      ADI R4, R4, #1      R4 = (0 + 1) = 1      0000000 100 100 001      0121
        X"0F24", --0011      SR R4, R4, R4      R4 = (1 >> 1) = 0x8000 0000111 100 100 100      0F24
        X"0ADB", --0100      ADD R3, R3, R3      R3 = (6 + 6) = 12      0000101 011 011 011      0ADB
        X"03D8", --0101      LD R7, Memory[R3]  R7 = Memory[12] = 0x00FF 0000001 111 011 000      03D8
        X"08D8", --0110      NOT R3, R3          R3 = (~12) = 0xFFFF 0000100 011 011 000      08D8
        X"06D8", --0111      INC R3, R3          4x(R3 = R3 + 1) = 0 0000011 011 011 000      06D8
        X"177C", --1000      BNEZ snl, 177C      0001011 111 000 110      177C
        X"3A00", --1001      stop B stop        State now = {R3==0 R4==0x8000 R7==0xFF} 0011101 000 000 000      3A00
        X"0000", --
        X"0000", --
        X"00FF", --(Memory[12])
        X"0000", --
        X"0000", --
        X"0000", --

        X"0000", X"0000", X"0000", X"0000", --x0010 - x001F

        ...

        X"0000", X"0000", X"0000", X"0000",
        X"0000", X"0000", X"0000", X"0000",
        X"0000", X"0000", X"0000", X"0000", --x01F0 - x01FF
        X"0000", X"0000", X"0000", X"0000",
        X"0000", X"0000", X"0000", X"0000",
        X"0000", X"0000", X"0000", X"0000" );
    variable addr:integer;

    begin -- the following type conversion function is in std_logic_arith
        snl <= unsigned(address);
        addr:= to_integer(snl(6 downto 0));

        if MemWrite ='1' then
            data_mem(addr):= write_data;
        end if;
        read_data<=data_mem(addr);

    end process;

end Behavioral;

```

Control Memory Behavioural

```

-- Engineer
-- Create Date:    17:54:17 03/29/2016
-- Module Name:    control_memory - Behavioral
-- Project Name:    CS2022 Computer Architecture 2016 Project 2
--

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity control_memory is
Port (
    MW : out std_logic;
    MM : out std_logic;
    RW : out std_logic;
    MD : out std_logic;
    FS : out std_logic_vector(4 downto 0);
    MB : out std_logic;
    TB : out std_logic;
    TA : out std_logic;
    TD : out std_logic;
    PL : out std_logic;
    PI : out std_logic;
    IL : out std_logic;
    MC : out std_logic;
    MS : out std_logic_vector(2 downto 0);
    NA : out std_logic_vector(7 downto 0);
    IN_CAR : in std_logic_vector(7 downto 0));
end control_memory;

architecture Behavioral of control_memory is
type mem_array is array(0 to 255) of std_logic_vector(27 downto 0);

--Instruction  Address  Next Address  . MS  MC.IL PI PL TD.TA TB MB . FS .MD RW MM MW  Code
-- ADI          00      IF -> C0      001  0 0 0 0 0 0 0 0 1 00010 0 1 0 0 = 0xC020224
-- LD           01      IF -> C0      001  0 0 0 0 0 0 0 0 0 00000 1 1 0 0 = 0xC02000C
-- ST           02      IF -> C0      001  0 0 0 0 0 0 0 0 0 00000 0 0 0 1 = 0xC020001
-- INC          03      IF -> C0      001  0 0 0 0 0 0 0 0 0 00001 0 1 0 0 = 0xC020014
-- NOT          04      TF -> C0      001  0 0 0 0 0 0 0 0 0 01110 0 1 0 0 = 0xC020084

-- LRI          06      LRI2-> 86      001  0 0 0 0 0 0 0 0 0 00000 1 1 0 0 = 0x862000C
-- SR           07      SR2 -> 87      111  0 0 0 0 0 1 0 0 0 00000 0 1 0 0 = 0x871004

-- BEQ          09      B -> 30      100  0 0 0 0 1 1 1 1 0 10000 0 1 0 0 = 0x0081D04
-- Catch        0A      IF -> C0      001  0 0 0 0 0 0 0 0 0 00000 0 0 0 0 = 0xC020000

-- BNZ          0B      B -> 30      111  0 0 0 0 0 0 0 0 0 00000 0 0 0 0 = 0x30E0000
-- Catch        0C      IF -> C0      001  0 0 0 0 0 0 0 0 0 00000 0 0 0 0 = 0xC020000

-- CMP          0D      IF -> C0      001  0 0 0 0 0 1 0 0 0 00101 0 1 0 0 = 0xC021054
-- LR           29      IF -> C0      001  0 0 0 0 0 0 0 0 0 00000 1 1 0 0 = 0xC02000C
-- B            30      IF -> C0      001  0 0 0 0 1 0 0 0 0 00000 0 0 0 0 = 0xC022000

-- LRI2         86      IF -> C0      001  0 0 0 0 0 0 0 1 0 0 00000 1 1 0 0 = 0xC02080C
-- SR2          87      SR3 -> 89      001  0 0 0 0 0 0 0 0 0 10100 0 1 0 0 = 0x8820144
-- SR3          88      SR2 -> 87      100  0 0 0 0 0 1 1 0 0 00110 0 1 0 0 = 0x8781864
-- Catch        89      IF -> C0      001  0 0 0 0 0 0 0 0 0 00000 0 0 0 0 = 0xC020000

-- IF           C0      EX0 -> C1      000  0 1 1 0 0 0 0 0 0 00000 0 0 1 0 = 0xC10C002
-- EX0          C1      -- -> 00      001  1 0 0 0 0 0 0 0 0 00000 0 0 0 0 = 0x0030000

begin

memory_m: process(IN_CAR)
variable control_mem : mem_array:=()

X"C020224", -- 0x00 ADI: Add immediate constant
X"C02000C", -- 0x01 LD: Load
X"C020001", -- 0x02 ST: Store
X"C020014", -- 0x03 INC: Increment
X"C020084", -- 0x04 NOT: Not
X"C020024", -- 0x05 ADD: Add
X"862000C", -- 0x06 LRI: Load into immediate register Micro-operation 1
X"871004", -- 0x07 SR: Shift Right Micro-operation 1
X"C020000", -- 0x08 Catch (to fall through to if shifted right by zero)
X"3080000", -- 0x09 BEQ: Branch if equal
X"C020000", -- 0x0A Catch (to fall through to if branch not taken)
X"30E0000", -- 0x0B BNZ: Branch if not zero
X"C020000", -- 0x0C Catch (to fall through to if branch not taken)
X"C021054", -- 0x0D CMP: Compare
X"0000000", -- 0x0E

...

X"0000000", -- 0x28
X"C02000C", -- 0x29 LR: Load
X"0000000", -- 0x2A
X"0000000", -- 0x2B
X"0000000", -- 0x2C
X"0000000", -- 0x2D
X"0000000", -- 0x2E
X"0000000", -- 0x2F

X"C022000", -- 0x30 B: Unconditional Branch
X"0000000", -- 0x31

...

```

Control Memory Test Bench

```

-- Engineer
-- Create Date: 12:38:54 04/01/2016
-- Module Name: U:/decoder_3cd9/control_memory_TestBench.vhd
-- Project Name: CS2022 Computer Architecture 2016 Project 2

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY control_memory_TestBench IS
END control_memory_TestBench;

ARCHITECTURE behavior OF control_memory_TestBench IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT control_memory
    PORT(
        MW : OUT std_logic;
        MM : OUT std_logic;
        RW : OUT std_logic;
        MD : OUT std_logic;
        FS : OUT std_logic_vector(4 downto 0);
        MB : OUT std_logic;
        TB : OUT std_logic;
        TA : OUT std_logic;
        TD : OUT std_logic;
        PL : OUT std_logic;
        PI : OUT std_logic;
        IL : OUT std_logic;
        MC : OUT std_logic;
        MS : OUT std_logic_vector(2 downto 0);
        NA : OUT std_logic_vector(7 downto 0);
        IN_CAR : IN std_logic_vector(7 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal IN_CAR : std_logic_vector(7 downto 0) := (others => '0');

    --Outputs
    signal MW : std_logic;
    signal MM : std_logic;
    signal RW : std_logic;
    signal MD : std_logic;
    signal FS : std_logic_vector(4 downto 0);
    signal MB : std_logic;
    signal TB : std_logic;
    signal TA : std_logic;
    signal TD : std_logic;
    signal PL : std_logic;
    signal PI : std_logic;
    signal IL : std_logic;
    signal MC : std_logic;
    signal MS : std_logic_vector(2 downto 0);
    signal NA : std_logic_vector(7 downto 0);

BEGIN


    -- Instantiate the Unit Under Test (UUT)
    uut: control_memory PORT MAP (
        MW => MW,
        MM => MM,
        RW => RW,
        MD => MD,
        FS => FS,
        MB => MB,
        TB => TB,
        TA => TA,
        TD => TD,
        PL => PL,
        PI => PI,
        IL => IL,
        MC => MC,
        MS => MS,
        NA => NA,
        IN_CAR => IN_CAR
    );

    -- Stimulus process
    stim_proc0: process
    begin
        --Test that accessing IF address gives out the IF code:
        -- Next Address MS MC IL PI PL TD TA TB MB FS MD RW MM MW
        -- C1 001 0 1 1 0 0 0 0 0 00000 0 0 1 0
        IN_CAR <= x"C0";
        wait for 100 ns;

        --Test that accessing B address gives out the B code:
        -- Next Address MS MC IL PI PL TD TA TB MB FS MD RW MM MW
        -- C0 001 0 0 0 1 0 0 0 0 00000 0 0 0 0
        IN_CAR <= x"30";
        wait;
    end process;

END;

```

 

Instruction Register Behavioural

```

-- Engineer:
-- Create Date:    19:48:00 03/29/2016
-- Module Name:    IR - Behavioral
-- Project Name:   CS2022 Computer Architecture 2016 Project 2

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity IR is
    Port ( data_in : in  STD_LOGIC_VECTOR (15 downto 0);
          IL : in  STD_LOGIC;
          Clk : in  STD_LOGIC;
          Opcode : out STD_LOGIC_VECTOR (6 downto 0);
          DR : out  STD_LOGIC_VECTOR (2 downto 0);
          SA : out  STD_LOGIC_VECTOR (2 downto 0);
          SB : out  STD_LOGIC_VECTOR (2 downto 0));
end IR;

```

architecture Behavioral of IR is

```

-- 16 bit Register
COMPONENT reg16
PORT(
    D : IN std_logic_vector(15 downto 0);
    load : IN std_logic;
    Clk : IN std_logic;
    Q : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

```

signal data_out : std_logic_vector(15 downto 0);

begin


```

-- register
reg: reg16 PORT MAP(
    D => data_in,
    load => IL,
    Clk => Clk,
    Q => data_out
);

Opcode<=data_out(15 downto 9);
DR<=data_out(8 downto 6);
SA<=data_out(5 downto 3);
SB<=data_out(2 downto 0);

```

end Behavioral;

 

Instruction Register Test Bench

```

-- Engineer:
-- Create Date:    20:01:03 03/29/2016
-- Module Name:    U:/decoder_3to8/IR_TestBench.vhd
-- Project Name:   CS2022 Computer Architecture 2016 Project 2
-- VHDL Test Bench Created by ISE for module: IR

```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

```

```

ENTITY IR_TestBench IS
END IR_TestBench;

```

ARCHITECTURE behavior OF IR_TestBench IS

-- Component Declaration for the Unit Under Test (UUT)

```

COMPONENT IR
PORT(
    data_in : IN std_logic_vector(15 downto 0);
    IL : IN std_logic;
    Clk : IN std_logic;
    Opcode : OUT std_logic_vector(6 downto 0);
    DR : OUT std_logic_vector(2 downto 0);
    SA : OUT std_logic_vector(2 downto 0);
    SB : OUT std_logic_vector(2 downto 0)
);
END COMPONENT;

```

```

--Inputs
signal data_in : std_logic_vector(15 downto 0) := (others => '0');
signal IL : std_logic := '0';
signal Clk : std_logic := '0';

```

```

--Outputs
signal Opcode : std_logic_vector(6 downto 0);
signal DR : std_logic_vector(2 downto 0);
signal SA : std_logic_vector(2 downto 0);
signal SB : std_logic_vector(2 downto 0);

```

```

-- Clock period definitions
constant Clk_period : time := 10 ns;

```

BEGIN

```

-- Instantiate the Unit Under Test (UUT)
uut: IR PORT MAP (
    data_in => data_in,
    IL => IL,
    Clk => Clk,
    Opcode => Opcode,
    DR => DR,
    SA => SA,
    SB => SB
);

```

```

-- Clock process definitions
Clk_process :process
begin
    Clk <= '0';
    wait for Clk_period/2;
    Clk <= '1';
    wait for Clk_period/2;
end process;

```

```

-- Stimulus process
stim_proc0: process
begin
    --Test Data being loaded in.
    --Opcode = 01000000, DR = 111, SA = 101, SB = 011.
    --Data in = 01000000 111 101 011, IL = 1.
    data_in <= "0100000011101011";
    IL <= '1';
    wait for Clk_period*2;

    --Test Data not being loaded in. (Therefore the Outputs are the same as the last test)
    --Opcode = 01000000, DR = 111, SA = 101, SB = 011.
    --Data in = 00111000 010 111 000, IL = 1.
    data_in <= "0011100001011000";
    IL <= '0';
    wait;
end process;

```

END;

Extend Behavioural

```

-----
-- Engine
-- Create Date:    18:38:47 03/31/2016
-- Module Name:    Extend - Behavioral
-- Project Name:    CS2022 Computer Architecture 2016 Project 2
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Extend is
    Port ( DR : in  STD_LOGIC_VECTOR (2 downto 0);
          SB : in  STD_LOGIC_VECTOR (2 downto 0);
          extension : out STD_LOGIC_VECTOR (15 downto 0));
end Extend;

architecture Behavioral of Extend is

begin
    extension(15 downto 6) <= "0000000000" when (DR(2)='0') else "1111111111";
    extension(5 downto 3) <= DR;
    extension(2 downto 0) <= SB;
end Behavioral;

```

Extend Test Bench

```

-----
-- Compan
-- Create Date:    18:50:37 03/31/2016
-- Module Name:    U:/decoder_3to8/Extend_TestBench.vhd
-- Project Name:    CS2022 Computer Architecture 2016 Project 2
-----

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Extend_TestBench IS
END Extend_TestBench;

ARCHITECTURE behavior OF Extend_TestBench IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT Extend
    PORT(
        DR : IN  std_logic_vector(2 downto 0);
        SB : IN  std_logic_vector(2 downto 0);
        extension : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal DR : std_logic_vector(2 downto 0) := (others => '0');
    signal SB : std_logic_vector(2 downto 0) := (others => '0');

    --Outputs
    signal extension : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Extend PORT MAP (
        DR => DR,
        SB => SB,
        extension => extension
    );

    -- Stimulus process
    stim_proc: process
    begin
        -- Test with most significant bit = 1
        DR <= "101";
        SB <= "010";
        -- Extension = 1111111111101010
        wait for 100 ns;

        -- Test with most significant bit = 0
        DR <= "011";
        SB <= "011";
        -- Extension = 0000000000011011
        wait;
    end process;

END;

```

Name	Value	0 ns	50 ns	100 ns	150 ns	200 ns	250 ns
dr[2:0]	011	101				011	
sb[2:0]	011	010				011	
extension[15:0]	0000000000001101	1111111111101010				0000000000011011	

Control Address Register Behavioural

```
-----
-- Engineer
-- Create Date:      20:46:25 03/29/2016
-- Module Name:      CAR - Behavioral
-- Project Name:      CS2022 Computer Architecture 2016 Project 2
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity CAR is
    Port ( data_in : in  STD_LOGIC_VECTOR (7 downto 0);
          reset : in  STD_LOGIC;
          Con : in  STD_LOGIC;
          Clk : in  STD_LOGIC;
          data_out : out  STD_LOGIC_VECTOR (7 downto 0));
end CAR;

architecture Behavioral of CAR is

    COMPONENT ripple_adder_16bit
    PORT(
        A : IN std_logic_vector(15 downto 0);
        B : IN std_logic_vector(15 downto 0);
        Cin : IN std_logic;
        S : OUT std_logic_vector(15 downto 0);
        Cout : OUT std_logic;
        Vout : OUT std_logic
    );
    END COMPONENT;

    -- 16 bit Register
    COMPONENT reg16
    PORT(
        D : IN std_logic_vector(15 downto 0);
        load : IN std_logic;
        Clk : IN std_logic;
        Q : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    signal increment : std_logic_vector(7 downto 0);
    signal unused : std_logic_vector (7 downto 0);
    signal current_val : std_logic_vector (15 downto 0);
    signal into_reg : std_logic_vector (15 downto 0);

begin

    -- ripple_adder_16bit
    adder: ripple_adder_16bit PORT MAP(
        A(7 downto 0) => current_val(7 downto 0),
        A(15 downto 8) => x"00",
        B => x"0001",
        Cin => '0',
        S(7 downto 0) => increment,
        s(15 downto 8) => unused
    );

    -- register
    reg: reg16 PORT MAP(
        D => into_reg,
        load => '1',
        Clk => Clk,
        Q => current_val
    );

    --into_reg(7 downto 0) <= x"C0" when reset='1' else data_in when Con = '1' else increment;
    into_reg(7 downto 0) <= data_in when Con = '1' else increment;
    into_reg(15 downto 8) <= x"00";
    data_out <= current_val(7 downto 0);

end Behavioral;
```

Control Address Register Test Bench

```

-----
-- Engineer:
-- Create Date:    21:07:45 03/29/2016
-- Module Name:    U:/decoder_3to8/CAR_TestBench.vhd
-- Project Name:    CS2022 Computer Architecture 2016 Project 2
-- VHDL Test Bench Created by ISE for module: CAR
-----

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY CAR_TestBench IS
END CAR_TestBench;

ARCHITECTURE behavior OF CAR_TestBench IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT CAR
    PORT(
        data_in : IN  std_logic_vector(7 downto 0);
        reset   : IN  std_logic;
        Clk     : IN  std_logic;
        Con     : IN  std_logic;
        data_out : OUT std_logic_vector(7 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal data_in : std_logic_vector(7 downto 0) := (others => '0');
    signal Con : std_logic := '0';
    signal Clk : std_logic := '0';
    signal reset : std_logic := '0';

    --Outputs
    signal data_out : std_logic_vector(7 downto 0);

    -- Clock period definitions
    constant Clk_period : time := 10 ns;

BEGIN


    -- Instantiate the Unit Under Test (UUT)
    uut: CAR PORT MAP (
        data_in => data_in,
        reset => reset,
        Clk => Clk,
        Con => Con,
        data_out => data_out
    );

    -- Clock process definitions
    Clk_process :process
    begin
        Clk <= '0';
        wait for Clk_period/2;
        Clk <= '1';
        wait for Clk_period/2;
    end process;

    -- Stimulus process
    stim_proc0: process
    begin
        --Load the CAR with the input (condition == 1)
        data_in <= "01000001";
        Con <= '1';
        reset <= '0';
        --data_out = 01000001
        wait for Clk_period*2;

        --Increment the CAR (condition == 0)
        data_in <= "01000001";
        Con <= '0';
        --data_out = 01000010
        wait;
    end process;

END;
```

 

Zero Fill Behavioural

```

-----
-- Engineer:
-- Create Date:    13:15:43 03/30/2016
-- Module Name:    zero_fill - Behavioral
-- Project Name:    CS2022 Computer Architecture 2016 Project 2
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity zero_fill is
    Port ( SB : in  STD_LOGIC_VECTOR (2 downto 0);
          constant_out : out STD_LOGIC_VECTOR (15 downto 0));
end zero_fill;

architecture Behavioral of zero_fill is

begin
    constant_out(2 downto 0) <= SB;
    constant_out(15 downto 3) <= "000000000000000";
end Behavioral;

```

Zero Fill Test Bench

```

-----
-- Engineer:
-- Create Date:    13:22:45 03/30/2016
-- Module Name:    U:/decoder_3to8/zero_fill_TestBench.vhd
-- Project Name:    CS2022 Computer Architecture 2016 Project 2
-- VHDL Test Bench Created by ISE for module: zero_fill
-----

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY zero_fill_TestBench IS
END zero_fill_TestBench;

ARCHITECTURE behavior OF zero_fill_TestBench IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT zero_fill
    PORT(
        SB : IN  std_logic_vector(2 downto 0);
        constant_out : OUT  std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal SB : std_logic_vector(2 downto 0) := (others => '0');

    --Outputs
    signal constant_out : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: zero_fill PORT MAP (
        SB => SB,
        constant_out => constant_out
    );

    -- Stimulus process
    stim_proc: process
    begin
        --Test with the constant as 5
        SB <= "101";
        wait for 100 ns;

        --Test with the constant as 0
        SB <= "000";
        wait for 100 ns;

        --Test with the constant as 2
        SB <= "010";
        wait;
    end process;

END;

```

